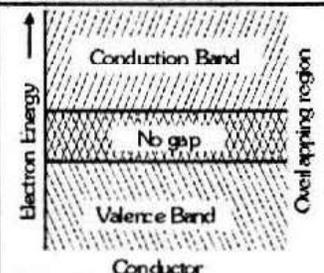
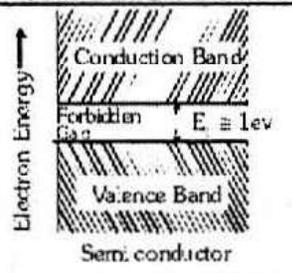
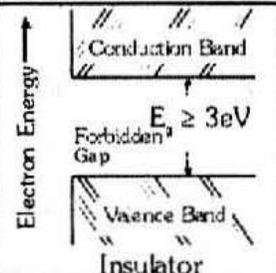


## SEMICONDUCTOR


### Comparison between conductor, semiconductor and insulator :

Properties	Conductor	Semiconductor	Insulator
Resistivity	$10^{-2} - 10^{-4} \Omega m$	$10^{-5} - 10^6 \Omega m$	$10^{11} - 10^{19} \Omega m$
Conductivity	$10^2 - 10^8 \text{ mho/m}$	$10^5 - 10^{-6} \text{ mho/m}$	$10^{-11} - 10^{-19} \text{ mho/m}$
Temp. Coefficient of resistance ( $\alpha$ )	Positive	Negative	Negative
Current	Due to free electrons	Due to electrons and holes	No current
Energy band diagram	 <p>Conductor</p>	 <p>Semiconductor</p>	 <p>Insulator</p>
Forbidden energy gap	$\approx 0 \text{ eV}$	$\approx 1 \text{ eV}$	$\geq 3 \text{ eV}$
Example	Pt, Al, Cu, Ag	Ge, Si, GaAs, GaF <sub>2</sub>	Wood, plastic, Diamond, Mica

- ◆ **Number of electrons reaching from valence band to conduction band**

$$n = AT^{3/2} e^{-\frac{\Delta E_g}{2kT}}$$

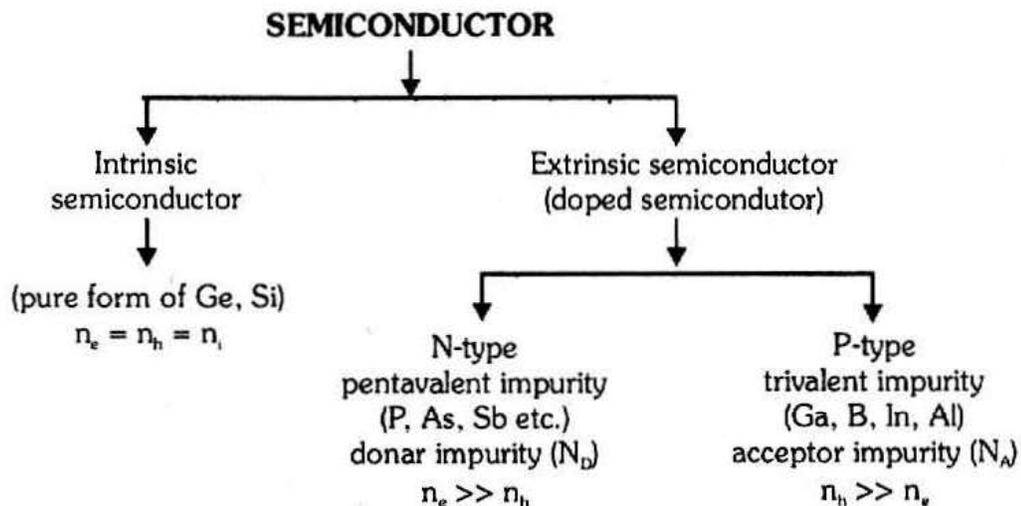- ◆ **Classification of Semiconductors :**





- ◆ **Mass-action law**  $n_i^2 = n_e \times n_h$ 
  - For N-type semiconductor  $n_e = N_D$
  - For P-type semiconductor  $n_h = N_A$
- ◆ **Conductivity**  $n_i e (\mu_e + \mu_h)$

Intrinsic Semiconductor	N-type (Pentavalent impurity)	P-type (Trivalent impurity)
Current due to electron and hole	Mainly due to electrons	Mainly due to holes
$n_e = n_h = n_i$	$n_h \ll n_e (N_D \approx n_e)$	$n_h \gg n_e (N_A \approx n_h)$
$I = I_e + I_h$	$I \approx I_e$	$I \approx I_h$
Entirely neutral	Entirely neutral	Entirely neutral
Quantity of electrons and holes are equal	Majority - Electrons Minority - Holes	Majority - Holes Minority - Electrons



### Comparison between Forward Bias and Reverse Bias

Forward Bias		Reverse Bias	
1	Potential Barrier reduces	1	Potential Barrier increases.
2	Width of depletion layer decreases	2	Width of depletion layer increases.
3	P-N jn. provide very small resistance	3	P-N jn. provide high resistance
4	Forward current flows in the circuit	4	Very small current flows.
5	Order of forward current is milli ampere.	5	Order of current is micro ampere for Ge or Nano ampere for Si.
6	Current flows mainly due to majority carriers.	6	Current flows mainly due to minority carriers.
7	Forward characteristic curves.	7	Reverse characteristic curve
8	Forward resistance : $R_f = \frac{\Delta V_f}{\Delta I_f} \approx 100\Omega$	8	Reverse resistance : $R_r = \frac{\Delta V_r}{\Delta I_r} \approx 10^6\Omega$
9	Order of knee or cut in voltage	9	Breakdown voltage
	Ge $\rightarrow$ 0.3 V		Ge $\rightarrow$ 25 V
	Si $\rightarrow$ 0.7 V		Si $\rightarrow$ 35 V
Special point : Generally $\frac{R_r}{R_f} = 10^3 : 1$ for Ge		$\frac{R_r}{R_f} = 10^4 : 1$ for Si	



• **Half wave rectifier**

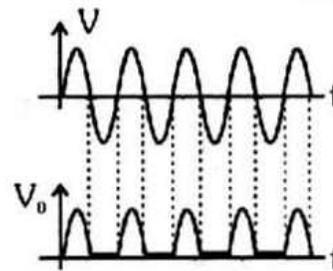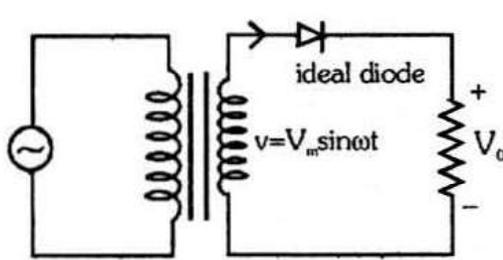

• **Centre - Tap Full wave Rectifier**

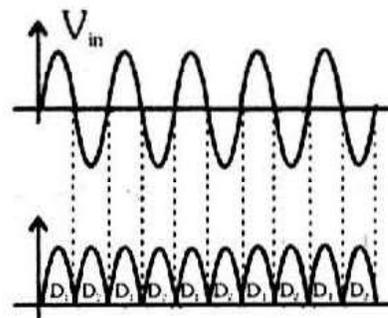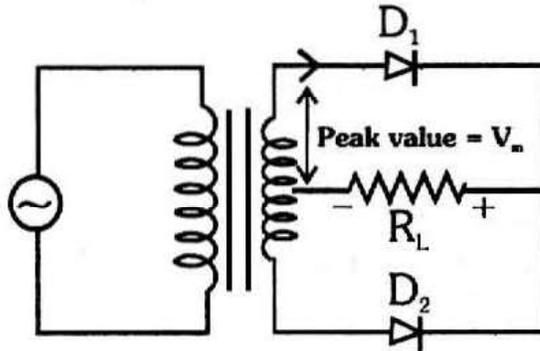

• **Full wave Bridge rectifier**

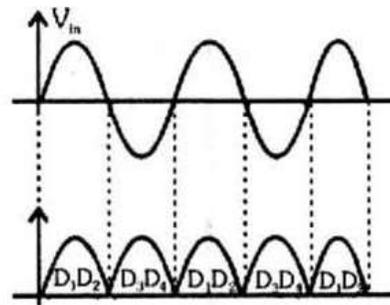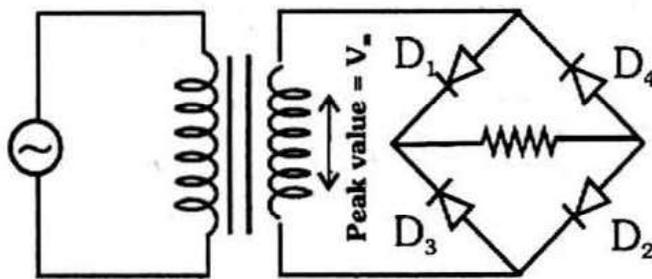

♦ **Form factor** =  $\frac{I_{rms}}{I_{dc}}$

□ For HWR (Half wave rectifier) Form factor =  $\frac{\pi}{2}$

□ For FWR (Full wave rectifier) Form factor =  $\frac{\pi}{2\sqrt{2}}$

♦ **Ripple factor**  $r = \frac{I_{ac}}{I_{dc}}$

□ For HWR  $r = 1.21$


□ For FWR  $r = 0.48$

♦ **Rectifier efficiency**  $\eta = \frac{P_{dc}}{P_{ac}} = \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_F + R_L)}$


□ For HWR  $\eta\% = \frac{40.6}{1 + \frac{R_F}{R_L}}$  & FWR  $\eta\% = \frac{81.2}{1 + \frac{R_F}{R_L}}$

♦ For transistor

$$I_E = I_B + I_C$$

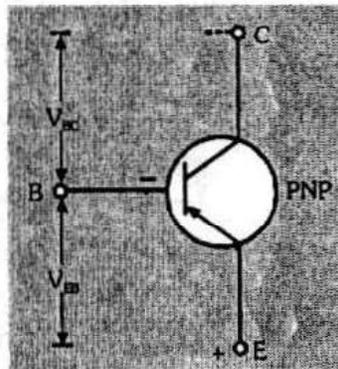

(a)

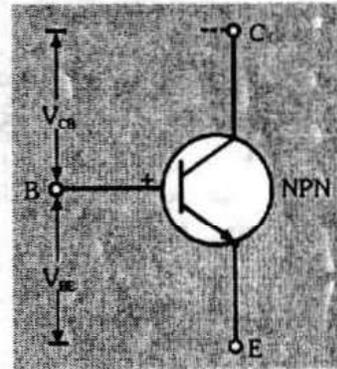

(b)

### Comparative study of transistor configurations


1. Common Base (CB)
2. Common Emitter (CE)
3. Common Collector (CC)

	CB	CE	CC
<b>Input Resistance</b>	Low (100 Ω)	High (750 Ω)	Very High $\cong 750 \text{ k}\Omega$
<b>Output resistance</b>	Very High	High	Low
<b>Current Gain</b>	( $A_i$ or $\alpha$ )	( $A_i$ or $\beta$ )	( $A_i$ or $\gamma$ )
	$\alpha = \frac{I_C}{I_E} < 1$	$\beta = \frac{I_C}{I_B} > 1$	$\gamma = \frac{I_E}{I_B} > 1$
<b>Voltage Gain</b>	$A_v = \frac{V_o}{V_i} = \frac{I_C R_L}{I_E R_i}$	$A_v = \frac{V_o}{V_i} = \frac{I_C R_L}{I_B R_i}$	$A_v = \frac{V_o}{V_i} = \frac{I_E R_L}{I_B R_i}$
	$A_v = \alpha \frac{R_L}{R_i} \cong 150$	$A_v = \beta \frac{R_L}{R_i} \cong 500$	$A_v = \gamma \frac{R_L}{R_i} < 1$
<b>Power Gain</b>	$A_p = \frac{P_o}{P_i} = \alpha^2 \frac{R_L}{R_i}$	$A_p = \frac{P_o}{P_i} = \beta^2 \frac{R_L}{R_i}$	$A_p = \frac{P_o}{P_i} = \gamma^2 \frac{R_L}{R_i}$
<b>Phase difference (between output and input)</b>	same phase	opposite phase	same phase
<b>Application</b>	For High Frequency	For Audible frequency	For Impedance Matching

♦ **Relation between  $\alpha$ ,  $\beta$  and  $\gamma$  :**  $\beta = \frac{\alpha}{1-\alpha}$ ,  $\gamma = 1 + \beta$ ,  $\gamma = \frac{1}{1-\alpha}$

♦ **Logic gates**


□ OR gate

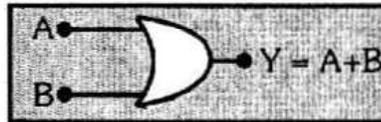


□ AND gate




□ NOT gate

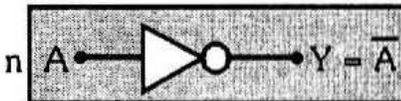


□ NOR gate

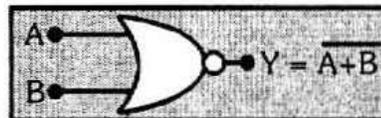


□ NAND gate

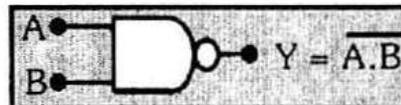

□ XOR gate

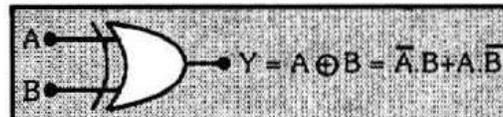

□ XNOR gate

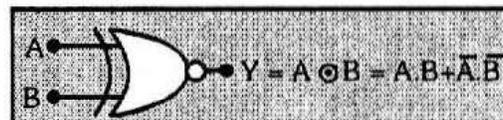

♦ **De Morgan's theorem**

$$\overline{A+B} = \bar{A} \cdot \bar{B}, \quad \overline{A \cdot B} = \bar{A} + \bar{B}$$

OR	AND	NOT
$A + 0 = A$	$A \cdot 0 = 0$	$A + \bar{A} = 1$
$A + 1 = 1$	$A \cdot 1 = A$	$A \cdot \bar{A} = 0$
$A + A = A$	$A \cdot A = A$	$\bar{\bar{A}} \cdot A = A$

## Important notes